

Juan Felipe Camargo Espinosa, Braian Alejandro Tuberquia Arciniegas

Universidad de Ibagué

2420182012estudiantesunibague.edu.co

24020182022@estudiantesunibague.edu.co

I. INTRODUCTION

A code was made for a line follower car in MPLAB assembly language, which consists of 5 sensors to identify the line where the car is going to travel, 3 LEDs, two yellow ones that indicate the direction where it is turning (left right) and a red one that indicates that the car is stopped.

II. THEORETICAL FRAMEWORK

In order to carry out the code we have to make a truth table for each sensor of the car and for each led. With this truth table made, we proceed to make a Karnaugh diagram and thus extract the function of each sensor and LED, and with this make the code in assembly language.

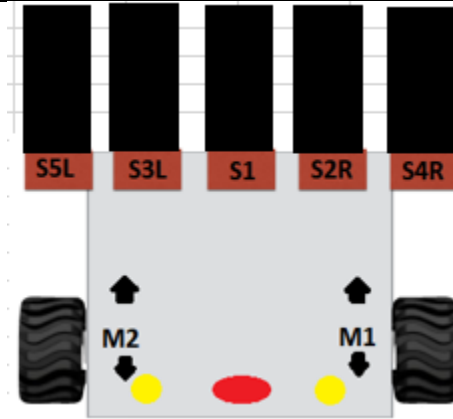


Fig. 1: Line follower trolley model

III. RESULTS

A truth table was made for each sensor and each led, taking into account what logical values we would assign to each sensor depending on the position of the line.

	S1	S2R	S3L	S4R	S5L	M1Forward
0	0	0	0	0	0	0
1	0	0	0	0	1	1
2	0	0	0	1	0	0
3	0	0	0	1	1	X
4	0	0	1	0	0	1
5	0	0	1	0	1	1
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	0
9	0	1	0	0	1	X
10	0	1	0	1	0	0
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	1
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	1
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	0
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	1
30	1	1	1	1	0	0
31	1	1	1	1	1	0

Date table 1: Truth table engine 1 forward

Taking into account the truth table, we do the Karnaugh map for engine 1 forward.

MOTOR 1 FORWARD								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110.	111.	101.	100.
00.	0	1	X	0	X	X	1	1
01.	0	X	X	0	X	X	X	X
11.	0	X	X	X	0	0	1	X
10.	1	X	X	X	X	X	X	1

$$F1 = S1 * \underline{S2R} + \underline{S3L} * S5L + S3L * \underline{S4R}$$

Fig 2 Karnaugh Map of Engine 1 Forward

	S1	S2R	S3L	S4R	S5L	M2 Forward
0	0	0	0	0	0	0
1	0	0	0	0	1	0
2	0	0	0	1	0	1
3	0	0	0	1	1	X
4	0	0	1	0	0	0
5	0	0	1	0	1	0
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	1
9	0	1	0	0	1	X
10	0	1	0	1	0	1
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	1
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	0
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	1
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	0
30	1	1	1	1	0	1
31	1	1	1	1	1	0

Date table 2: Truth table engine 2 Forward

Taking into account the truth table, we do the Karnaugh map for engine 2 forward.

MOTOR 2 FORWARD								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110.	111.	101.	100.
00.	0	0	X	1	X	X	0	0
01.	1	X	X	1	X	X	X	X
11.	1	X	X	X	1	0	0	X
10.	1	X	X	X	X	X	X	0

$$F2 = S4R * \underline{S5L} + \underline{S1} * S2R + S1 * \underline{S3L}$$

Fig. 3 Karnaugh Map of Engine 2 Forward

	S1	S2R	S3L	S4R	S5L	M1 Reverse
0	0	0	0	0	0	1
1	0	0	0	0	1	0
2	0	0	0	1	0	1
3	0	0	0	1	1	X
4	0	0	1	0	0	0
5	0	0	1	0	1	0
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	0
9	0	1	0	0	1	X
10	0	1	0	1	0	1
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	0
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	0
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	0
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	0
30	1	1	1	1	0	0
31	1	1	1	1	1	0

Date table 3: Truth table engine 1 Reverse

Taking into account the truth table, we do the Karnaugh map for engine 1 reverse.

MOTOR 1 REVERSE								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110.	111.	101.	100.
00.	1	0	X	1	X	X	0	0
01.	0	X	X	1	X	X	X	X
11.	0	X	X	X	0	0	0	X
10.	0	X	X	X	X	X	X	0

$$F3 = \underline{S3L} * S4R + \underline{S1} * \underline{S2R} * \underline{S3L} * \underline{S4R} * \underline{S5L}$$

Fig. 4 Karnaugh Map of Engine 1 Reverse

	S1	S2R	S3L	S4R	S5L	M2 Reverse
0	0	0	0	0	0	1
1	0	0	0	0	1	1
2	0	0	0	1	0	0
3	0	0	0	1	1	X
4	0	0	1	0	0	0
5	0	0	1	0	1	1
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	0
9	0	1	0	0	1	X
10	0	1	0	1	0	0
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	0
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	0
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	0
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	0
30	1	1	1	1	0	0
31	1	1	1	1	1	0

Date table 4: Truth table engine 2
Reverse

Taking into account the truth table, we do the Karnaugh map for engine 2 Reverse.

MOTOR 2 REVERSE								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110	111	101	100
00.	1	1	X	0	X	X	1	0
01.	0	X	X	0	X	X	X	X
11.	0	X	X	X	0	0	0	X
10.	0	X	X	X	X	X	X	0

$$F4 = \underline{S1} * \underline{S5L} + \underline{S1} * \underline{S2R} * \underline{S3L} * \underline{S4R}$$

Fig 5 Karnaugh Map of Engine 2
Reverse

	S1	S2R	S3L	S4R	S5L	Led 1(RIGHT)
0	0	0	0	0	0	0
1	0	0	0	0	1	0
2	0	0	0	1	0	1
3	0	0	0	1	1	X
4	0	0	1	0	0	0
5	0	0	1	0	1	0
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	1
9	0	1	0	0	1	X
10	0	1	0	1	0	1
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	0
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	0
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	1
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	0
30	1	1	1	1	0	1
31	1	1	1	1	1	0

Date table 5: Truth table Led1
RIGHT(Yellow)

Taking into account the truth table, we do the Karnaugh map for Led1 RIGHT (Yellow).

LED 1 RIGHT								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110	111	101	100
00.	0	0	X	1	X	X	0	0
01.	1	X	X	1	X	X	X	X
11.	1	X	X	X	1	0	0	X
10.	0	X	X	X	X	X	X	0

$$F5 = \underline{S4R} * \underline{S5L} + \underline{S2R} * \underline{S3L}$$

Fig 6: Karnaugh map for Led1
RIGHT(Yellow)

	S1	S2R	S3L	S4R	S5L	*Led2(LEFT)
0	0	0	0	0	0	0
1	0	0	0	0	1	1
2	0	0	0	1	0	0
3	0	0	0	1	1	X
4	0	0	1	0	0	1
5	0	0	1	0	1	1
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	0
9	0	1	0	0	1	X
10	0	1	0	1	0	0
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	0
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	1
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	0
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	1
30	1	1	1	1	0	0
31	1	1	1	1	1	0

Date table 6: Truth table Led2
LEFT(Yellow)

Taking into account the truth table, we
do the Karnaugh map for Led2 LEFT
(Yellow).

LED 2 LEFT								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110.	111.	101.	100.
00.	0	1	X	0	X	X	1	1
01.	0	X	X	0	X	X	X	X
11.	0	X	X	X	0	0	1	X
10.	0	X	X	X	X	X	X	1

$$F6 = \underline{S3L} * S5L + S3L * \underline{S4R}$$

Fig 7: Karnaugh map for Led2
LEFT(Yellow)

	S1	S2R	S3L	S4R	S5L	L-STOP
0	0	0	0	0	0	1
1	0	0	0	0	1	0
2	0	0	0	1	0	0
3	0	0	0	1	1	X
4	0	0	1	0	0	0
5	0	0	1	0	1	0
6	0	0	1	1	0	X
7	0	0	1	1	1	X
8	0	1	0	0	0	0
9	0	1	0	0	1	X
10	0	1	0	1	0	0
11	0	1	0	1	1	X
12	0	1	1	0	0	X
13	0	1	1	0	1	X
14	0	1	1	1	0	X
15	0	1	1	1	1	X
16	1	0	0	0	0	0
17	1	0	0	0	1	X
18	1	0	0	1	0	X
19	1	0	0	1	1	X
20	1	0	1	0	0	0
21	1	0	1	0	1	X
22	1	0	1	1	0	X
23	1	0	1	1	1	X
24	1	1	0	0	0	0
25	1	1	0	0	1	X
26	1	1	0	1	0	X
27	1	1	0	1	1	X
28	1	1	1	0	0	X
29	1	1	1	0	1	0
30	1	1	1	1	0	0
31	1	1	1	1	1	1

Date table 6: Truth table Led-
STOP(Red)

Taking into account the truth table,
we do the Karnaugh map for Led-
STOP (Red)

LED- STOP								
S1,S2R,S3L,S4R,S5L	000.	001.	011.	010.	110.	111.	101.	100.
00.	1	0	X	0	X	X	0	0
01.	0	X	X	0	X	X	X	X
11.	0	X	X	X	0	1	0	X
10.	0	X	X	X	X	X	X	0

$$F7 = \underline{S1} * \underline{S2R} * \underline{S3L} * \underline{S4R} * \underline{S5L} + S4R * S5L$$

Fig 7: Karnaugh map for Led-
STOP(Red)

V. CONCLUSIONS

A good handling of assembly language was learned for the line follower solution, a good analysis for the sensors and values that we gave to them and to perform Karnaugh diagrams again for their solution to these sensor analyzes.

VI. REFERENCES

- [1]
<https://ww1.microchip.com/downloads/en/devicedoc/39582b.pdf>
- [2]
<https://www.ti.com/lit/ds/symlink/l293.pdf>